
CS1050 Computer Organization and Digital Design

Lab 9-10 – Nanoprocessor Design Competition

Name	Index Number
Ranathunga N. D.	200517U
Keerthichandra H. M. P. M.	200304N
Marasinghe M. M. R. S.	200382A
Vihidun D. P. T.	200682T
Marium M. S. S.	200384G

Lab Task:

In this Lab, we were assigned to design and simulate a Nanoprocessor to execute several Assembly operations. Nanoprocessor was developed using components mentioned below.

Program Counter

- Specifically designed for this Lab

Program ROM

- designed by modifying the LUT in Lab 07

Register Bank

- Specifically designed for this Lab
- Register bank consists of seven 4-bit registers
- The Assembly Language code was converted to a 12-bit signal and stored in the Register Bank.

4-bit Add/Sub Unit

- designed by modifying 4-bit RCA in Lab 03
- The Add/Sub unit is capable of adding and subtracting two 4-bit numbers, using Two's complement method.

3-bit Adder -

- An optimized version was specifically designed for this Lab

8-way 4-bit Mux

- An optimized version was specifically designed for this Lab

2-way 3-bit Mux

- An optimized version was specifically designed for this Lab

Load Select Mux

- An optimized version was specifically designed for this Lab

Several buses were used to connect components together, including Instruction Bus(12-bit), Data bus(4-bit), Address to Jump(3-bit).

Vivado Simulator tool was used to verify the functionality of the Nanoprocessor, before implementing into BASYS3 board.

Assembly Code and its Machine Code:

- **Assembly Program**

Binary instructions stored in the program counter consist of 12 bits. Those instructions have the following structure.

Instruction	Description	Format (12-bit instruction)
MOVI R, <i>d</i>	Move immediate value <i>d</i> to register R, i.e., $R \leftarrow d$ $R \in [0, 7], d \in [0, 15]$	1 0 R R R 0 0 0 d d d d
ADD Ra, Rb	Add values in registers Ra and Rb and store the result in Ra, i.e., $Ra \leftarrow Ra + Rb$ $Ra, Rb \in [0, 7]$	0 0 Ra Ra Ra Rb Rb Rb 0 0 0 0
NEG R	2's complement of registers R, i.e., $R \leftarrow -R$ $R \in [0, 7]$	0 1 R R R 0 0 0 0 0 0 0
JZR R, d	Jump if value in register R is 0, i.e., If $R == 0$ $PC \leftarrow d$; Else $PC \leftarrow PC + 1$; $R \in [0, 7], d \in [0, 7]$	1 1 R R R 0 0 0 0 d d d

- **Assembly Code**

The assembly code stored in the program counter is given below.

```

----- Operations -----
"100010001010", --- MOVI R1, 10 ; R1 <= 10
"100100000001", --- MOVI R2, 1 ; R2 <= 1
"010100000000", --- NEG R2 ; R2 <= -R2
"000010100000", --- ADD R1, R2 ; R1 <= R1 + R2
"110010000000", --- JZR R1, 7 ; If R1 = 0 jump to line 7
"110000000011" --- JZR R0, 3 ; If R0 = 0 jump to line 3

```

Program ROM:

VHDL Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;

entity ProgramROM is
    Port ( MemSelect : in STD_LOGIC_VECTOR (2 downto 0);
          I : out STD_LOGIC_VECTOR (11 downto 0));
end ProgramROM;


architecture Behavioral of ProgramROM is
    type rom_type is array(0 to 5) of std_logic_vector(11 downto 0);
    signal ProROM : rom_type := (
        ----- Operations -----
        "100010001010", --- MOVI R1, 10 ; R1 <= 10
        "100100000001", --- MOVI R2, 1 ; R2 <= 1
        "010100000000", --- NEG R2 ; R2 <= -R2
        "000010100000", --- ADD R1, R2 ; R1 <= R1 + R2
        "110010000000", --- JZR R1, 7 ; If R1 = 0 jump to line 7
        "110000000011" --- JZR R0, 3 ; If R0 = 0 jump to line 3
    );

begin
    I <= ProROM(to_integer(unsigned(MemSelect)));

end Behavioral;

```

Schematic Diagram

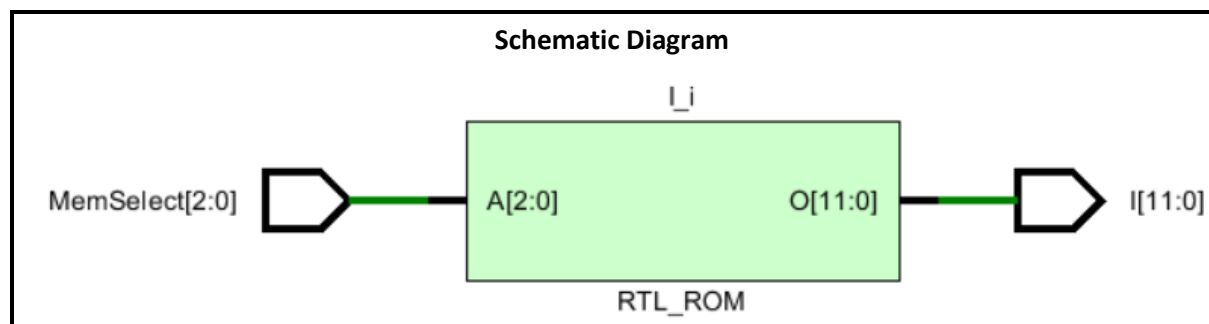

Program Counter:

VHDL Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Counter is
    Port ( Clk : in STD_LOGIC;
          Reset : in STD_LOGIC;
          D : in STD_LOGIC_VECTOR(2 downto 0);
          Q : out STD_LOGIC_VECTOR(2 downto 0));
end Counter;

```

```

architecture Behavioral of Counter is

component Reg_3bit
    Port ( D : in STD_LOGIC_VECTOR (2 downto 0);
          En : in STD_LOGIC;
          Clk : in STD_LOGIC;
          Q : out STD_LOGIC_VECTOR (2 downto 0));
end component;

signal dd: std_logic_vector (2 downto 0);
signal qq: std_logic_vector (2 downto 0);


begin

reg_0: Reg_3bit
    PORT MAP(
        Clk => Clk,
        En => '1',
        Q => Q,
        D => dd
    );

with Reset select dd <= d when '0',
                  d when 'U',
                  "000" when others;

end Behavioral;

```

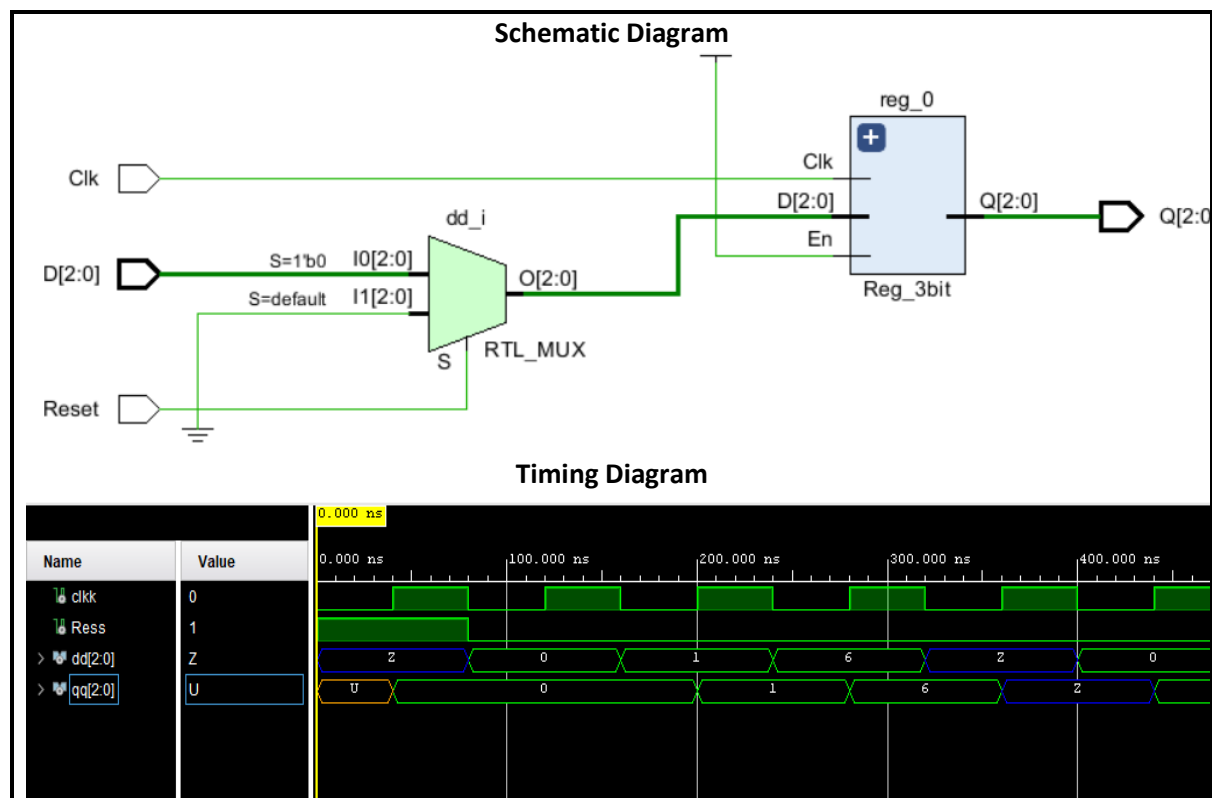

3-bit Adder:

VHDL Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity RCA is
    Port (Y : in STD_LOGIC_VECTOR (2 downto 0);
          S : out STD_LOGIC_VECTOR (2 downto 0);
          Cin : in STD_LOGIC;
          Cout : out STD_LOGIC);
end RCA;

architecture Behavioral of RCA is

    component FA
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          C_in : in STD_LOGIC;
          S : out STD_LOGIC;
          C_out : out STD_LOGIC);
    end component;

    signal FA_cout : STD_LOGIC_VECTOR (1 downto 0);

begin

    FA_0: FA

    PORT MAP(
    A=>'1',
    B=>Y(0),
    C_in=>Cin,
    S=>S(0),
    C_out=>FA_cout(0)
    );

    FA_1: FA

    PORT MAP(
    A=>'0',
    B=>Y(1),
    C_in=>FA_cout(0),
    S=>S(1),
    C_out=>FA_cout(1)
    );

    FA_2: FA

    PORT MAP(
    A=>'0',
    B=>Y(2),

```

```

C_in=>FA_cout(1),
S=>S(2),
C_out=>Cout
);


```

```

end Behavioral;

```

Schematic Diagram

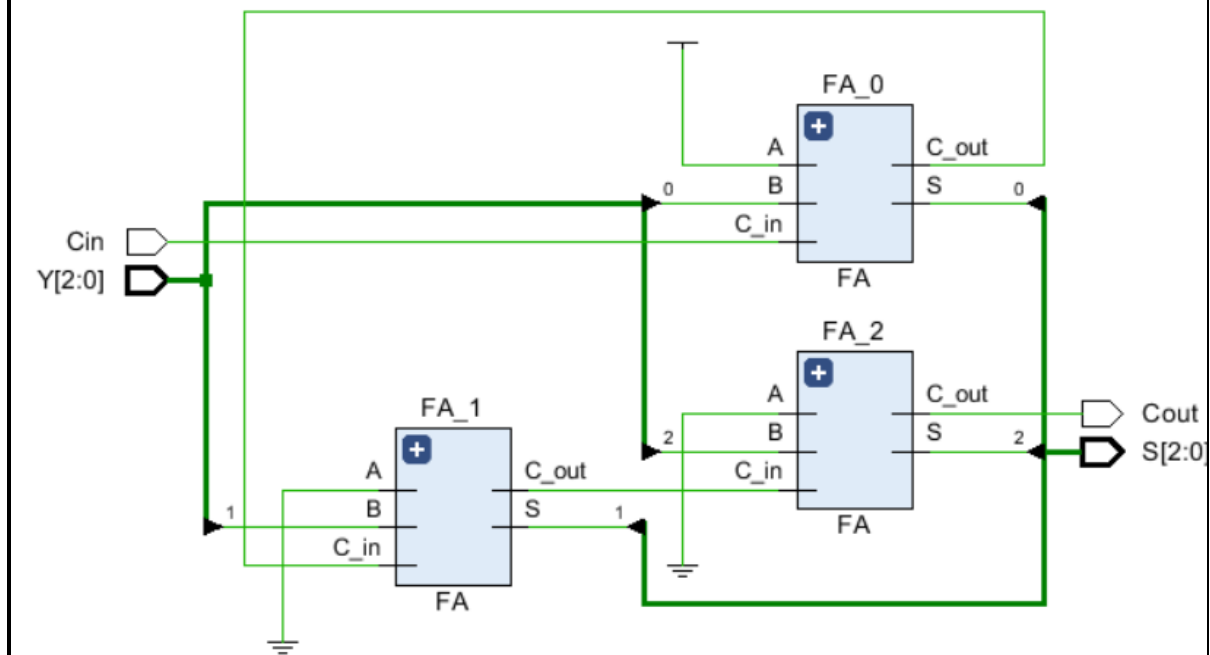

Timing Diagram



Instruction Decoder:

VHDL Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Instruction_Decoder is
    Port ( instruction : in STD_LOGIC_VECTOR (11 downto 0);
          reg_jump : in STD_LOGIC_VECTOR (3 downto 0);
          reg_en : out STD_LOGIC_VECTOR (2 downto 0);
          load_sel : out STD_LOGIC;
          im_val : out STD_LOGIC_VECTOR (3 downto 0);
          reg_sel_0 : out STD_LOGIC_VECTOR (2 downto 0);
          reg_sel_1 : out STD_LOGIC_VECTOR (2 downto 0);
          sub_sel : out STD_LOGIC;
          jmp_flag : out STD_LOGIC;
          jmp_address : out STD_LOGIC_VECTOR (2 downto 0));
end Instruction_Decoder;

architecture Behavioral of Instruction_Decoder is

    component Decoder_2_to_4
        Port ( I : in STD_LOGIC_VECTOR (1 downto 0);
              Y : out STD_LOGIC_VECTOR (3 downto 0);
              EN : in STD_LOGIC);
    end component;

    component Tri_state_buffer3
        Port ( A : in STD_LOGIC_VECTOR (2 downto 0);
              Y : out STD_LOGIC_VECTOR (2 downto 0);
              EN : in STD_LOGIC);
    end component;

    signal ADD, MOVI, NEG, JZR: STD_LOGIC;
    signal ADD_NEG, ADD_NEG_JZR: STD_LOGIC;
    signal reg_sel_0_activate, reg_sel_1_activate: STD_LOGIC_VECTOR (2
downto 0);

begin

    Decoder_2_to_4_0: Decoder_2_to_4
        PORT MAP(
            I => instruction(11 downto 10),
            EN => '1',
            Y(3) => ADD,
            Y(2) => MOVI,
            Y(1) => NEG,
            Y(0) => JZR
        );

    reg_en <= instruction(9 downto 7);
    load_sel <= not MOVI;
    im_val <= instruction(3 downto 0);

    ADD_NEG <= ADD or NEG;

```

```

ADD_NEG_JZR <= ADD_NEG or JZR;

reg_sel_1_activate <= (ADD_NEG, ADD_NEG, ADD_NEG);
reg_sel_0_activate <= (ADD_NEG_JZR, ADD_NEG_JZR, ADD_NEG_JZR);

reg_sel_0 <= instruction(9 downto 7) and reg_sel_0_activate;
reg_sel_1 <= instruction(6 downto 4) and reg_sel_1_activate;


sub_sel <= NEG;

jmp_flag <= JZR and not(reg_jump(0) or reg_jump(1) or reg_jump(2)
or reg_jump(3));
jmp_address <= instruction(2 downto 0);


end Behavioral;

```

Schematic Diagram

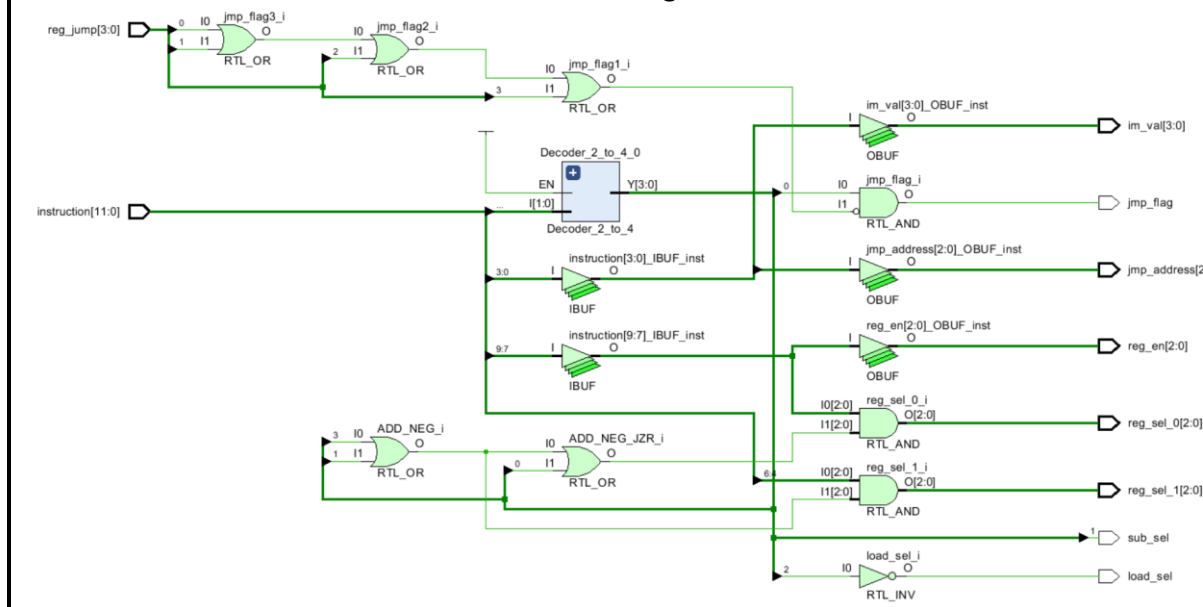

Timing Diagram

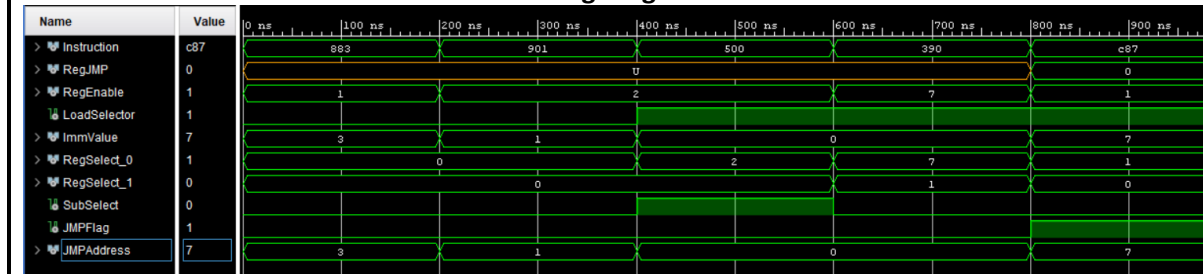

2-way 3-bit Mux:

VHDL Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux_2way_3bit is
    Port ( JmpAddress : in STD_LOGIC_VECTOR (2 downto 0);
          NextAddress : in STD_LOGIC_VECTOR (2 downto 0);
          JmpFlag : in STD_LOGIC;
          MuxOut : out STD_LOGIC_VECTOR (2 downto 0));
end mux_2way_3bit;

architecture Behavioral of mux_2way_3bit is


begin

with JmpFlag select MuxOut <= NextAddress when '0',
                    JmpAddress when '1',
                    nextaddress when others;


end Behavioral;

```

Schematic Diagram

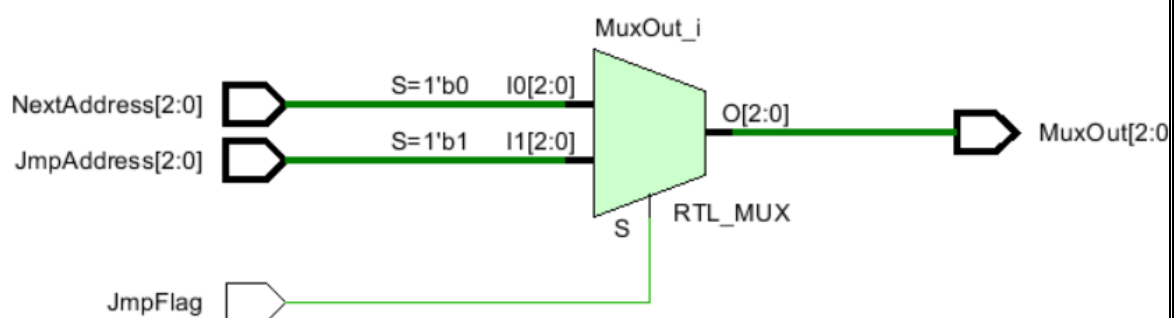

Timing Diagram

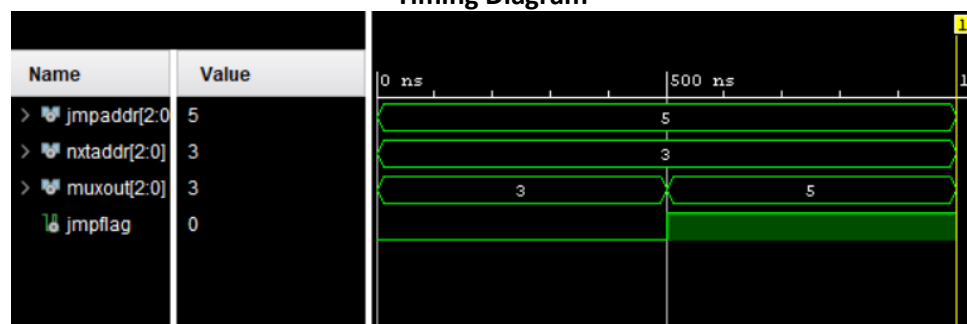

8-way 4-bit Mux:

VHDL Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux_8way_4bit is
    Port ( RegSel : in STD_LOGIC_VECTOR (2 downto 0);
          MuxOut : out STD_LOGIC_VECTOR (3 downto 0);
          D0 : in STD_LOGIC_VECTOR (3 downto 0);
          D1 : in STD_LOGIC_VECTOR (3 downto 0);
          D2 : in STD_LOGIC_VECTOR (3 downto 0);
          D3 : in STD_LOGIC_VECTOR (3 downto 0);
          D4 : in STD_LOGIC_VECTOR (3 downto 0);
          D5 : in STD_LOGIC_VECTOR (3 downto 0);
          D6 : in STD_LOGIC_VECTOR (3 downto 0);
          D7 : in STD_LOGIC_VECTOR (3 downto 0));
end mux_8way_4bit;

architecture Behavioral of mux_8way_4bit is


begin


with RegSel select MuxOut <= D0 when "000",
                           D1 when "001",
                           D2 when "010",
                           D3 when "011",
                           D4 when "100",
                           D5 when "101",
                           D6 when "110",
                           D7 when others;

end Behavioral;

```

Schematic Diagram

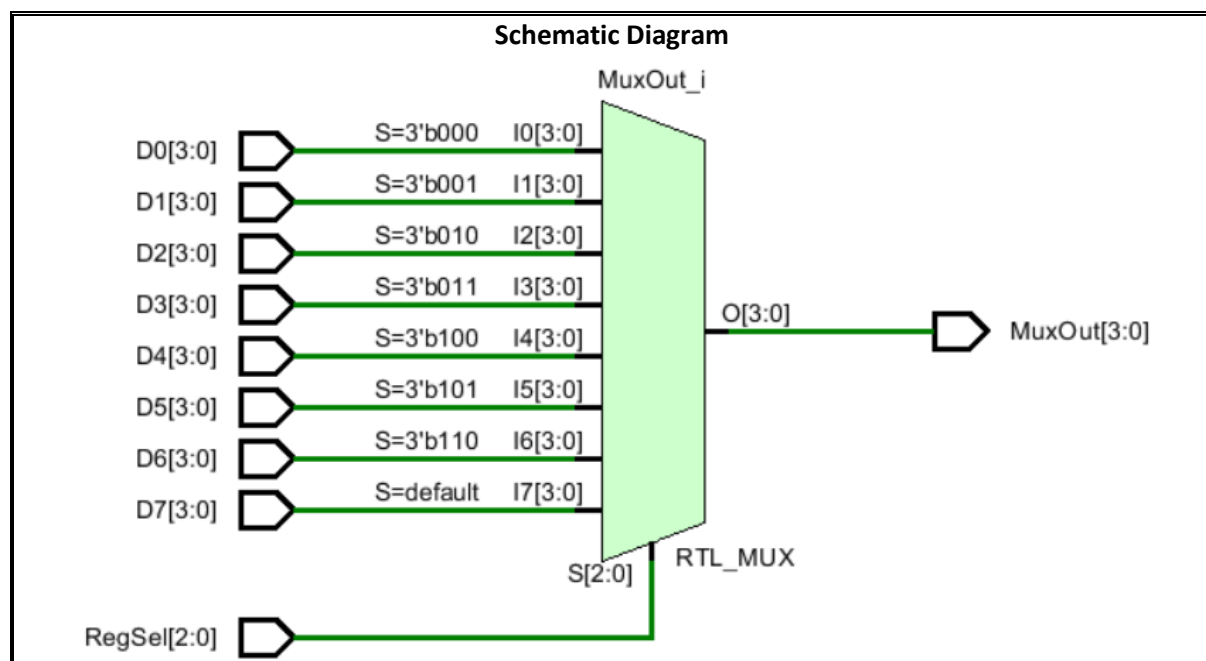

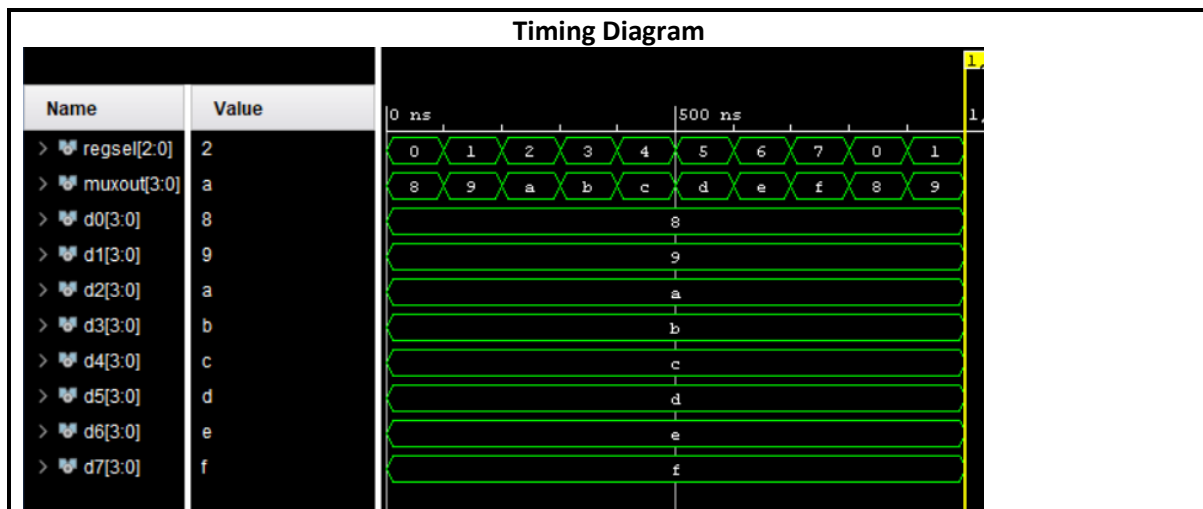

Load select Mux:

VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux_LoadSelect is
    Port ( LoadSel : in STD_LOGIC;
          AUresult : in STD_LOGIC_VECTOR (3 downto 0);
          ImmediateVal : in STD_LOGIC_VECTOR (3 downto 0);
          MuxOut : out STD_LOGIC_VECTOR (3 downto 0));
end mux_LoadSelect;


architecture Behavioral of mux_LoadSelect is


begin

with LoadSel select MuxOut <= ImmediateVal when '0',
                        AUresult when '1',
                        "ZZZZ" when others;

end Behavioral;
```

Schematic Diagram

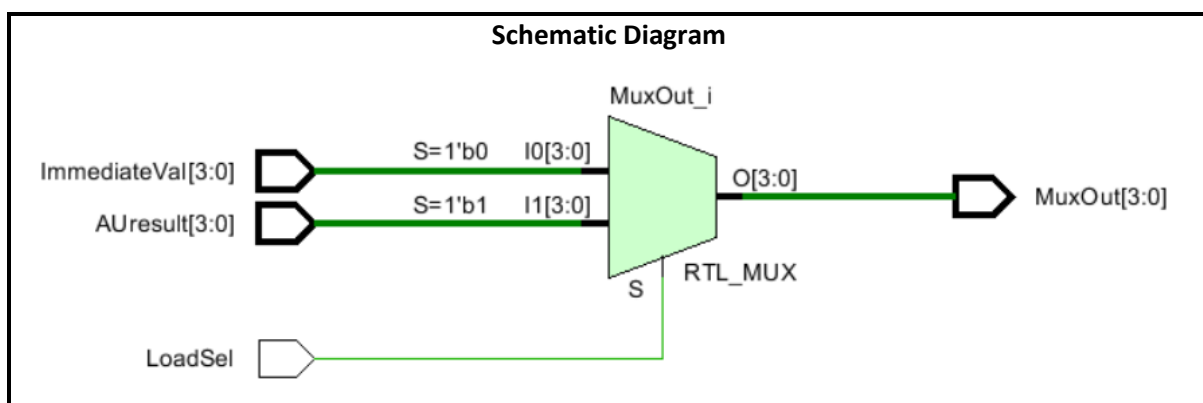

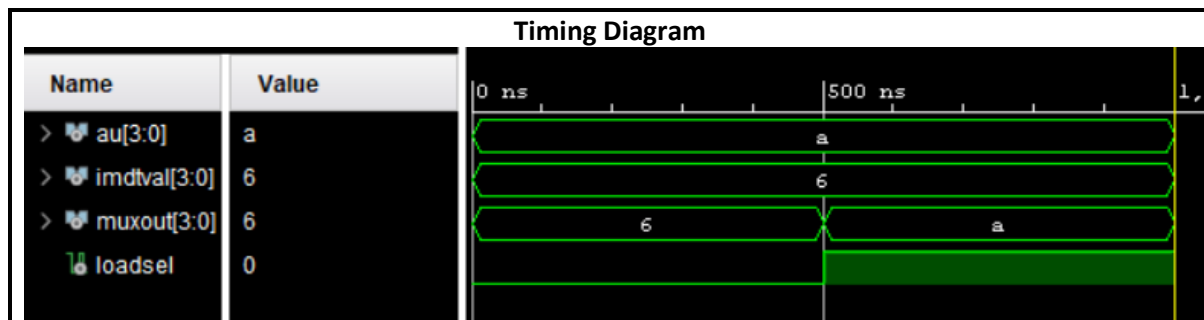

ADD_SUB Unit:

VHDL Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ADD_SUB is
    Port ( CTR : in STD_LOGIC;
          A0 : in STD_LOGIC;
          B0 : in STD_LOGIC;
          CTR_0 : in STD_LOGIC;
          C : out STD_LOGIC;
          S0 : out STD_LOGIC);
end ADD_SUB;

architecture Behavioral of ADD_SUB is
    component FA
        port (
            A : in STD_LOGIC;
            B : in STD_LOGIC;
            C_in : in STD_LOGIC;
            C_out : out STD_LOGIC;
            S : out STD_LOGIC
        );
    end component;


    signal B0_1: STD_LOGIC;

begin
    FA_1 : FA
    PORT MAP(
        A => A0,
        B => B0_1,
        C_in => CTR,
        C_out => C,
        S => S0
    );

    B0_1 <= CTR_0 XOR B0;

end Behavioral;

```

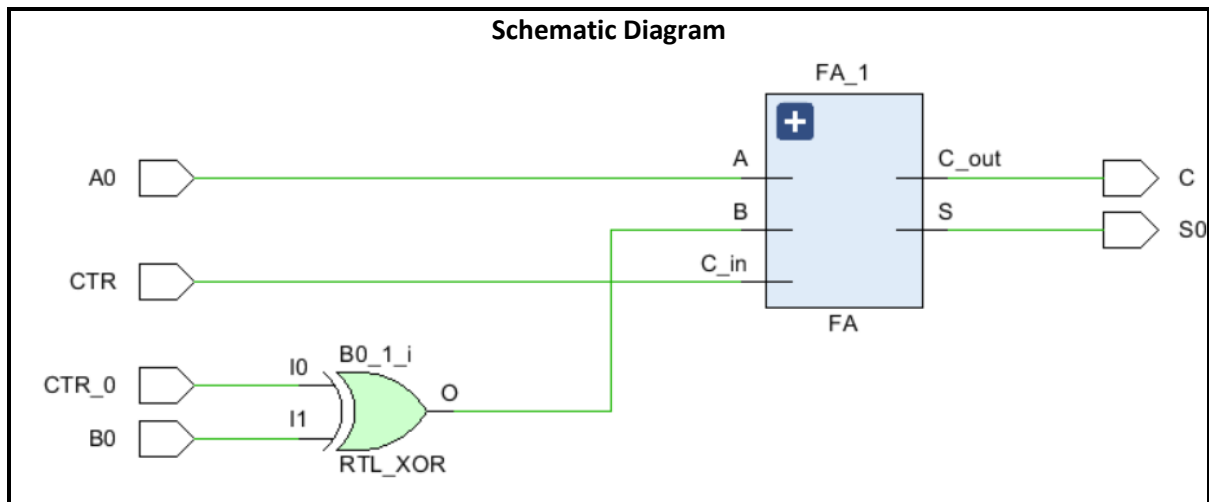

4-bit RC Add/Sub Unit:

VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity RCA_S is
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);
          CTR_in : in STD_LOGIC;
          C_out : out STD_LOGIC;
          S : out STD_LOGIC_VECTOR (3 downto 0);
          Zero: out STD_LOGIC);
end RCA_S;

architecture Behavioral of RCA_S is

    component ADD_SUB
        Port ( CTR : in STD_LOGIC;
              A0 : in STD_LOGIC;
              B0 : in STD_LOGIC;
              CTR_0 : in STD_LOGIC;
              C : out STD_LOGIC;
              S0 : out STD_LOGIC);
    end component;

    signal C0,C1,C2,C3, overflow : STD_LOGIC;
    signal AA, NEG: STD_LOGIC_VECTOR (3 downto 0);
    signal ss: STD_LOGIC_VECTOR (3 downto 0);
begin

    NEG <= (CTR_in, CTR_in, CTR_in, CTR_in);
    AA <= A and not NEG;

    ADD_SUB0 : ADD_SUB
        PORT MAP(
            CTR => CTR_in,
            A0 => AA(0),
            B0 => B(0),
```

```

        CTR_0 => CTR_in,
        C => C0,
        S0 => Ss(0)
    );

ADD_SUB1 : ADD_SUB
    PORT MAP(
        CTR => C0,
        A0 => AA(1),
        B0 => B(1),
        CTR_0 => CTR_in,
        C => C1,
        S0 => Ss(1)
    );

ADD_SUB2 : ADD_SUB
    PORT MAP(
        CTR => C1,
        A0 => AA(2),
        B0 => B(2),
        CTR_0 => CTR_in,
        C => C2,
        S0 => Ss(2)
    );


ADD_SUB3 : ADD_SUB
    PORT MAP(
        CTR => C2,
        A0 => AA(3),
        B0 => B(3),
        CTR_0 => CTR_in,
        C => C3,
        S0 => Ss(3)
    );


zero <= not Ss(0) and not ss(1) and not ss(2) and not ss(3);
overflow <= not CTR_in and (A(3) XNOR B(3)) and (A(3) XOR ss(3));
with overflow select s <= ('0', ss(2), ss(1), ss(0)) when '1',
                        ss when others;

C_Out <= overflow;
end Behavioral;

```

Schematic Diagram

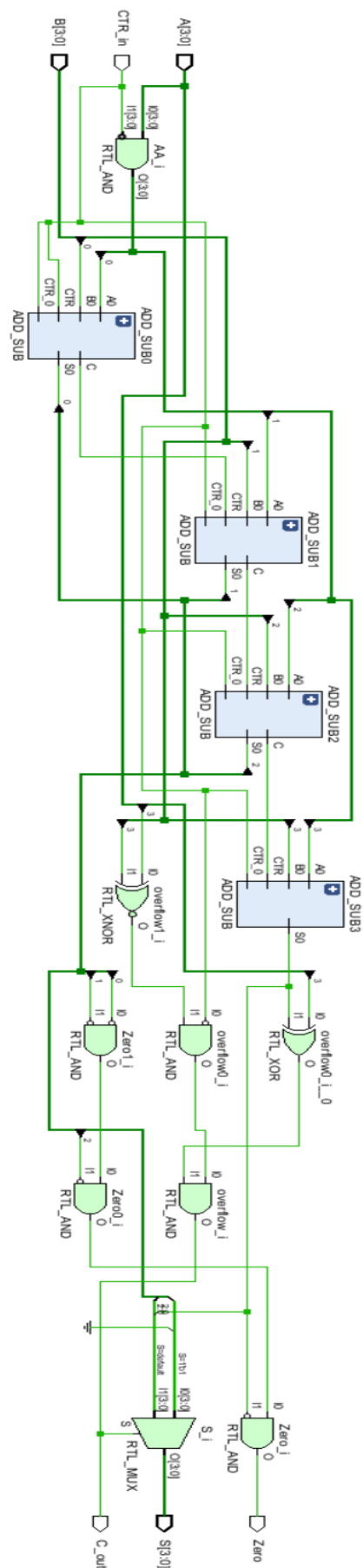

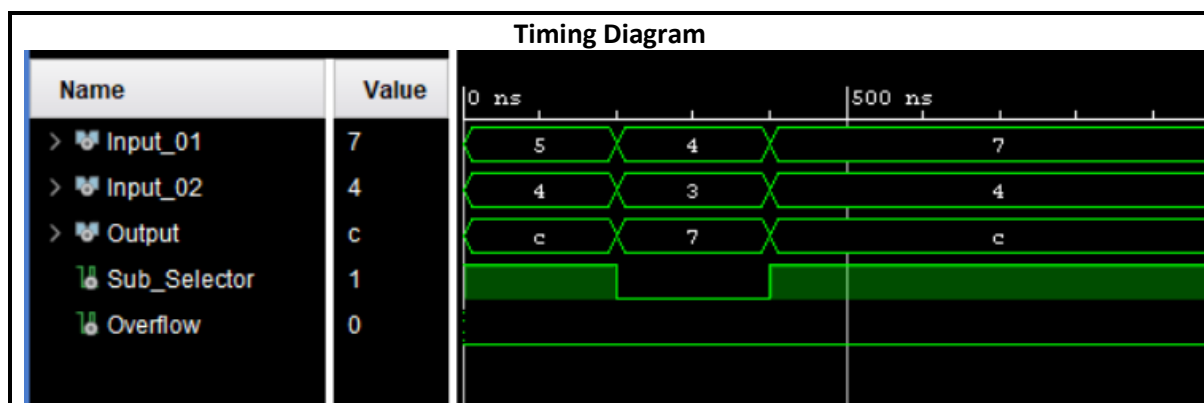


Register:

VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Reg is
    Port ( D : in STD_LOGIC_VECTOR (3 downto 0);
          En : in STD_LOGIC;
          Reset : in STD_LOGIC;
          Clk : in STD_LOGIC;
          Q : out STD_LOGIC_VECTOR (3 downto 0));
end Reg;

architecture Behavioral of Reg is
begin
    process(Clk) begin
        if (rising_edge(Clk)) then --respond when clock rises
            if Reset = '1' then
                Q <= "0000";
            elsif En = '1' then      -- Enable should be set
                Q <= D;
            end if;
        end if;
    end process;
end Behavioral;
```

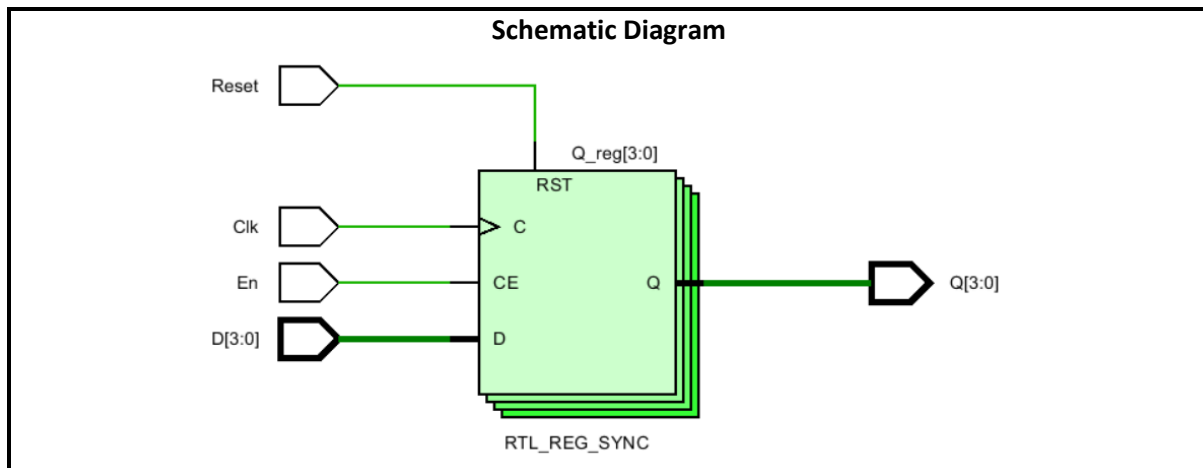3-8 Decoder:

VHDL Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Decoder_3_to_8 is
    Port ( I : in STD_LOGIC_VECTOR (2 downto 0);
          EN : in STD_LOGIC;
          Y : out STD_LOGIC_VECTOR (7 downto 0));
end Decoder_3_to_8;

architecture Behavioral of Decoder_3_to_8 is
    component decoder_2_to_4
        Port ( I : in STD_LOGIC_VECTOR (1 downto 0);
              Y : out STD_LOGIC_VECTOR (3 downto 0);
              EN : in STD_LOGIC);
    end component;

    signal I0,I1 : STD_LOGIC_VECTOR (1 downto 0);
    signal Y0,Y1 : STD_LOGIC_VECTOR (3 downto 0);
    signal en0,en1,I2 : STD_LOGIC;

begin

    Decoder_2_to_4_0 : Decoder_2_to_4
        port map(
            I => I0,
            EN => en0,
            Y => Y0
        );

    Decoder_2_to_4_1 : Decoder_2_to_4
        port map(
            I => I1,
            EN => en1,
            Y => Y1
        );

    en0 <= NOT(I(2)) AND EN;
    en1 <= I(2) AND EN;
    I0 <= I(1 downto 0);

```


```

I1 <= I(1 downto 0);
--I2 <= I(2);
Y(3 downto 0) <= Y0;
Y(7 downto 4) <= Y1;

end Behavioral;

```

Schematic Diagram

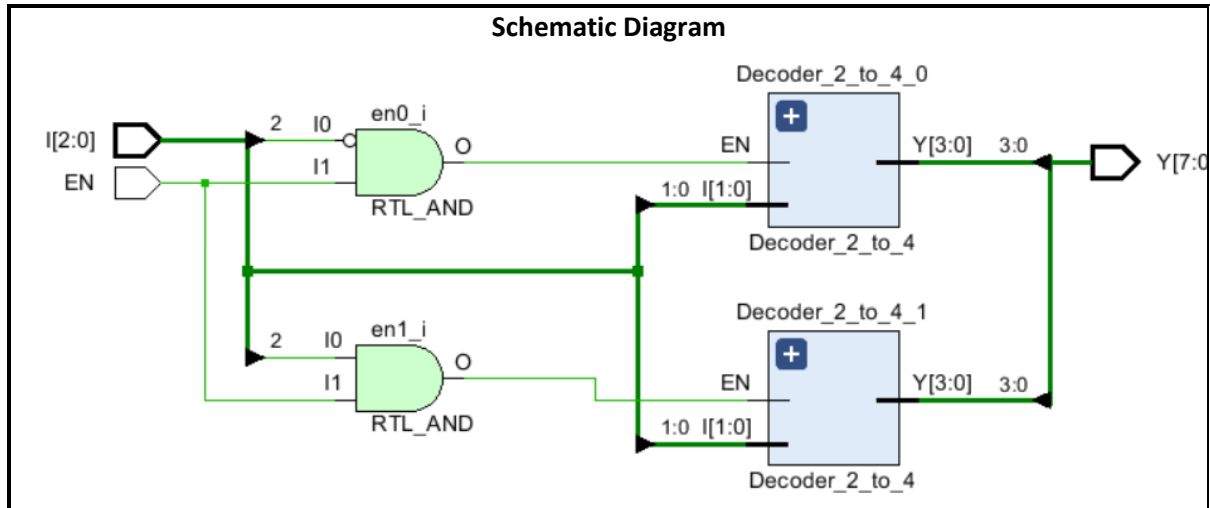

Register Bank:

VHDL Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity RegBank is
    Port ( Clk : in STD_LOGIC;
          Reset : in STD_LOGIC;
          RegEn : in STD_LOGIC_VECTOR (2 downto 0);
          DataIn : in STD_LOGIC_VECTOR (3 downto 0);
          DataBus0 : out STD_LOGIC_VECTOR (3 downto 0);
          DataBus1 : out STD_LOGIC_VECTOR (3 downto 0);
          DataBus2 : out STD_LOGIC_VECTOR (3 downto 0);
          DataBus3 : out STD_LOGIC_VECTOR (3 downto 0);
          DataBus4 : out STD_LOGIC_VECTOR (3 downto 0);
          DataBus5 : out STD_LOGIC_VECTOR (3 downto 0);
          DataBus6 : out STD_LOGIC_VECTOR (3 downto 0);
          DataBus7 : out STD_LOGIC_VECTOR (3 downto 0)
    );
end RegBank;

architecture Behavioral of RegBank is

    component Reg
        Port (D : in STD_LOGIC_VECTOR (3 downto 0);
             En : in STD_LOGIC;
             Reset : in STD_LOGIC;
             Clk : in STD_LOGIC;

```

```
        Q : out STD_LOGIC_VECTOR (3 downto 0));
end component;

component Decoder_3_to_8
    Port ( I : in STD_LOGIC_VECTOR (2 downto 0);
          EN : in STD_LOGIC;
          Y : out STD_LOGIC_VECTOR (7 downto 0));
end component;

signal DecOut: STD_LOGIC_VECTOR (7 downto 0);

begin

dec_3_to_8_0: Decoder_3_to_8
    PORT MAP(
        EN => '1',
        I => RegEn,
        Y => DecOut
    );

reg_0: Reg
    PORT MAP(
        D => DataIn,
        Q => DataBus0,
        En => DecOut(0),
        Clk => Clk,
        reset => reset
    );

reg_1: Reg
    PORT MAP(
        D => DataIn,
        Q => DataBus1,
        En => DecOut(1),
        Clk => Clk,
        reset => reset
    );

reg_2: Reg
    PORT MAP(
        D => DataIn,
        Q => DataBus2,
        En => DecOut(2),
        Clk => Clk,
        reset => reset
    );


reg_3: Reg
    PORT MAP(
        D => DataIn,
        Q => DataBus3,
        En => DecOut(3),
        Clk => Clk,
        reset => reset
    );
```

```
reg_4: Reg
  PORT MAP (
    D => DataIn,
    Q => DataBus4,
    En => DecOut(4),
    Clk => Clk,
    reset => reset
  );

reg_5: Reg
  PORT MAP (
    D => DataIn,
    Q => DataBus5,
    En => DecOut(5),
    Clk => Clk,
    reset => reset
  );

reg_6: Reg
  PORT MAP (
    D => DataIn,
    Q => DataBus6,
    En => DecOut(6),
    Clk => Clk,
    reset => reset
  );

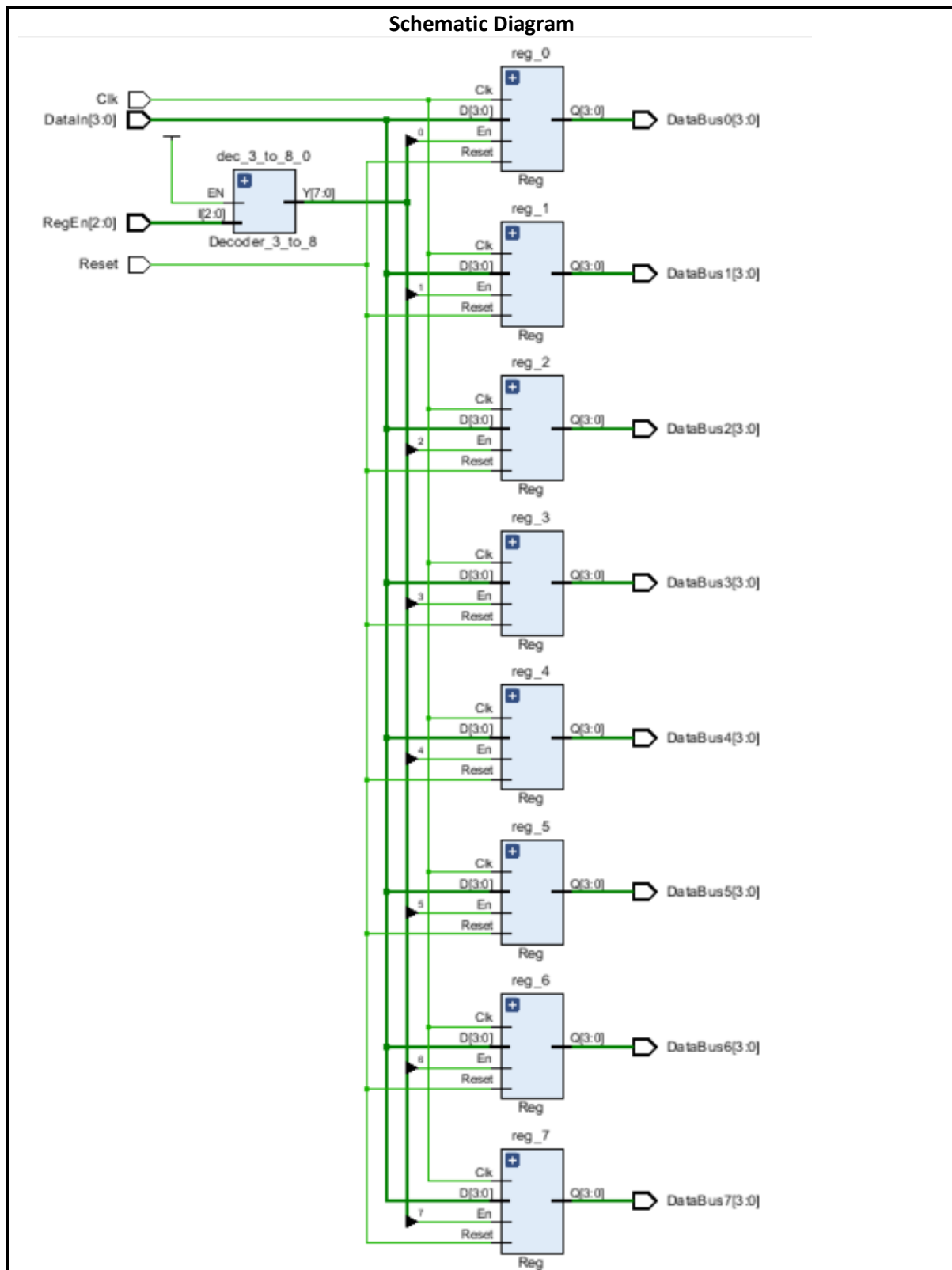reg_7: Reg
  PORT MAP (
    D => DataIn,
    Q => DataBus7,
    En => DecOut(7),
    Clk => Clk,
    reset => reset
  );
end Behavioral;
```



Nanoprocessor:

VHDL Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Nanoprocessor is
    Port ( Clock : in STD_LOGIC;
          Reset : in STD_LOGIC;
          Overflow : out STD_LOGIC;
          Zero : out STD_LOGIC);
end Nanoprocessor;

architecture Behavioral of Nanoprocessor is

    component Instruction_Decoder
        Port ( instruction : in STD_LOGIC_VECTOR (11 downto 0);
              reg_jump : in STD_LOGIC_VECTOR (3 downto 0);
              reg_en : out STD_LOGIC_VECTOR (2 downto 0);
              load_sel : out STD_LOGIC;
              im_val : out STD_LOGIC_VECTOR (3 downto 0);
              reg_sel_0 : out STD_LOGIC_VECTOR (2 downto 0);
              reg_sel_1 : out STD_LOGIC_VECTOR (2 downto 0);
              sub_sel : out STD_LOGIC;
              jmp_flag : out STD_LOGIC;
              jmp_address : out STD_LOGIC_VECTOR (2 downto 0));
    end component;

    component ProgramROM
        Port ( MemSelect : in STD_LOGIC_VECTOR (2 downto 0);
              I : out STD_LOGIC_VECTOR (11 downto 0));
    end component;

    component RegBank
        Port ( Clk : in STD_LOGIC;
              Reset : in STD_LOGIC;
              RegEn : in STD_LOGIC_VECTOR (2 downto 0);
              DataIn : in STD_LOGIC_VECTOR (3 downto 0);
              DataBus0 : out STD_LOGIC_VECTOR (3 downto 0);
              DataBus1 : out STD_LOGIC_VECTOR (3 downto 0);
              DataBus2 : out STD_LOGIC_VECTOR (3 downto 0);
              DataBus3 : out STD_LOGIC_VECTOR (3 downto 0);
              DataBus4 : out STD_LOGIC_VECTOR (3 downto 0);
              DataBus5 : out STD_LOGIC_VECTOR (3 downto 0);
              DataBus6 : out STD_LOGIC_VECTOR (3 downto 0);
              DataBus7 : out STD_LOGIC_VECTOR (3 downto 0)
            );
    end component;

    component Counter
        Port ( Clk : in STD_LOGIC;
              Reset : in STD_LOGIC;
              D : in STD_LOGIC_VECTOR (2 downto 0);
              Q : out STD_LOGIC_VECTOR (2 downto 0));
    end component;

```

```

component RCA_S
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);
          CTR_in : in STD_LOGIC;
          C_out : out STD_LOGIC;
          S : out STD_LOGIC_VECTOR (3 downto 0);
          Zero : out STD_LOGIC);
end component;

component RCA
    Port ( Y : in STD_LOGIC_VECTOR (2 downto 0);
          S : out STD_LOGIC_VECTOR (2 downto 0);
          Cin : in STD_LOGIC;
          Cout : out STD_LOGIC);
end component;

component mux_2way_3bit
    Port ( JmpAddress : in STD_LOGIC_VECTOR (2 downto 0);
          NextAddress : in STD_LOGIC_VECTOR (2 downto 0);
          JmpFlag : in STD_LOGIC;
          MuxOut : out STD_LOGIC_VECTOR (2 downto 0));
end component;

component mux_8way_4bit
    Port ( RegSel : in STD_LOGIC_VECTOR (2 downto 0);
          MuxOut : out STD_LOGIC_VECTOR (3 downto 0);
          D0 : in STD_LOGIC_VECTOR (3 downto 0);
          D1 : in STD_LOGIC_VECTOR (3 downto 0);
          D2 : in STD_LOGIC_VECTOR (3 downto 0);
          D3 : in STD_LOGIC_VECTOR (3 downto 0);
          D4 : in STD_LOGIC_VECTOR (3 downto 0);
          D5 : in STD_LOGIC_VECTOR (3 downto 0);
          D6 : in STD_LOGIC_VECTOR (3 downto 0);
          D7 : in STD_LOGIC_VECTOR (3 downto 0));
end component;

component mux_LoadSelect
    Port ( LoadSel : in STD_LOGIC;
          AUresult : in STD_LOGIC_VECTOR (3 downto 0);
          ImmediateVal : in STD_LOGIC_VECTOR (3 downto 0);
          MuxOut : out STD_LOGIC_VECTOR (3 downto 0));
end component;

component Slow_Clk
    Port ( Clk_in : in STD_LOGIC;
          Clk_out : out STD_LOGIC);
end component;

--Signals
signal Instruction_Bus: std_logic_vector (11 downto 0);
signal reg_check_jump, imm_val, from_asUnit, to_reg_bank:
std_logic_vector (3 downto 0);
signal addr_to_jump, reg_select0, reg_select1, reg_enable,
memory_select, to_pc, from_rca: std_logic_vector (2 downto 0);
signal jump_flag, add_sub_sel, load_selector, slw_clk,

```

```

RCA_Overflow: std_logic;

signal dbus0, dbus1, dbus2, dbus3, dbus4, dbus5, dbus6, dbus7:
std_logic_vector (3 downto 0);
signal to_asUnit_0, to_asUnit_1: std_logic_vector (3 downto 0);

begin

Instruction_Decoder_0: Instruction_decoder
  PORT MAP(
    instruction => Instruction_Bus,
    jmp_flag => jump_flag,
    jmp_address => addr_to_jump,
    sub_sel => add_sub_sel,
    load_sel => load_selector,
    im_val => imm_val,
    reg_sel_0 => reg_select0,
    reg_sel_1 => reg_select1,
    reg_en => reg_enable,
    reg_jump => reg_check_jump
  );

programROM_0: ProgramROM
  PORT MAP(
    MemSelect => memory_select,
    I => Instruction_Bus
  );

program_counter: Counter
  PORT MAP(
    Clk => slw_clk,
    Reset => Reset,
    D => to_pc,
    Q => memory_select
  );

Rca_0: RCA
  PORT MAP(
    Y => memory_select,
    S => from_rca,
    Cin => '0',
    Cout => RCA_Overflow
  );

mux_2_3: mux_2way_3bit
  PORT MAP(
    JmpAddress => addr_to_jump,
    NextAddress => from_rca,
    JmpFlag => jump_flag,
    MuxOut => to_pc
  );

muw0: mux_LoadSelect
  PORT MAP(
    LoadSel => load_selector,


```




```
        AUresult => from_asUnit,  
        ImmediateVal => imm_val,  
        MuxOut => to_reg_bank  
    );  
  
reg_bank: RegBank  
    PORT MAP(  
        Clk => slw_clk,  
        Reset => Reset,  
        RegEn => reg_enable,  
        DataIn => to_reg_bank,  
        DataBus0 => dbus0,  
        DataBus1 => dbus1,  
        DataBus2 => dbus2,  
        DataBus3 => dbus3,  
        DataBus4 => dbus4,  
        DataBus5 => dbus5,  
        DataBus6 => dbus6,  
        DataBus7 => dbus7  
    );  
  
mux_8_4_0: mux_8way_4bit  
    PORT MAP(  
        RegSel => reg_select0,  
        MuxOut => to_asUnit_1,  
        D0 => dbus0,  
        D1 => dbus1,  
        D2 => dbus2,  
        D3 => dbus3,  
        D4 => dbus4,  
        D5 => dbus5,  
        D6 => dbus6,  
        D7 => dbus7  
    );  
  
mux_8_4_1: mux_8way_4bit  
    PORT MAP(  
        RegSel => reg_select1,  
        MuxOut => to_asUnit_0,  
        D0 => dbus0,  
        D1 => dbus1,  
        D2 => dbus2,  
        D3 => dbus3,  
        D4 => dbus4,  
        D5 => dbus5,  
        D6 => dbus6,  
        D7 => dbus7  
    );  
  
rca_s_0: RCA_S  
    PORT MAP(  
        A => to_asUnit_0,  
        B => to_asUnit_1,  
        CTR_in => add_sub_sel,  
        C_out => Overflow,
```

```
        S => from_asUnit,  
        Zero => Zero  
    );  
  
slow_clk_0: Slow_Clk  
    PORT MAP(  
        Clk_in => Clock,  
        Clk_out => slw_clk  
    );  
  
reg_check_jump <= to_asUnit_0;  
  
end Behavioral;
```

Schematic Diagram

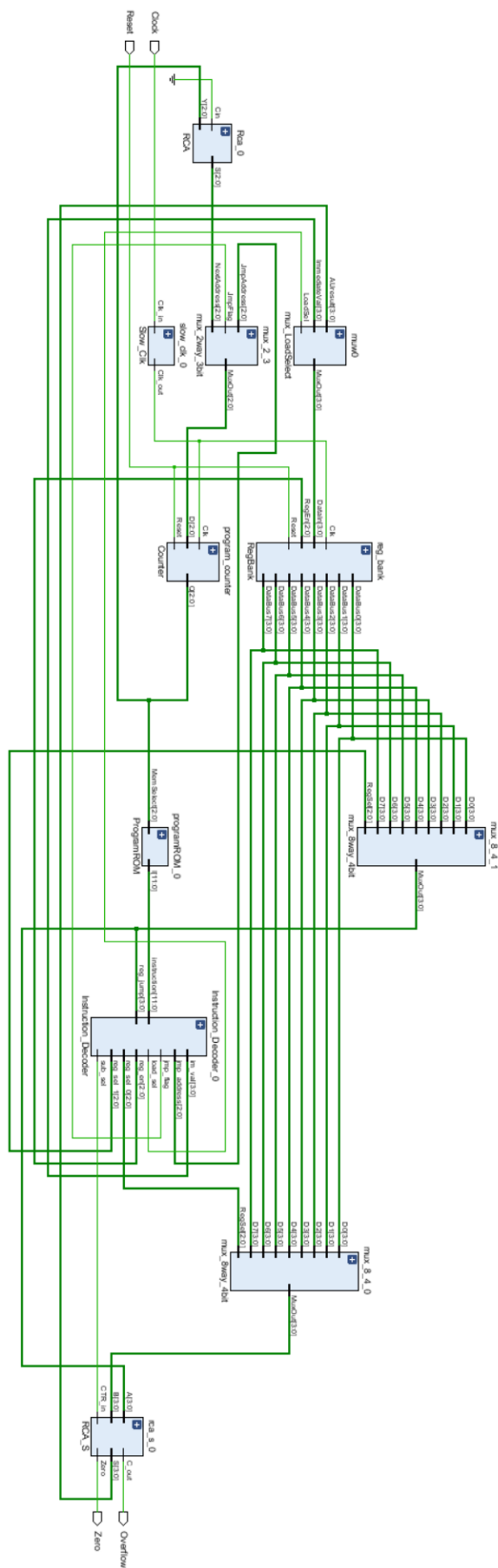

 

Conclusion:

- This nanoprocessor can be improved further by adding new components and improving the current components.
- We can increase the number range which we can execute mathematical operations using this nanoprocessor by increasing the width of the busses and other components.
- Instruction decoder plays a huge role in the nano processor because it is the component which activates the relevant components and busses to execute the instructions.
- We can optimize the nanoproceesor to give the best performance in the following way,
 - ❖ Improving the Add/Subtract unit to handle NEG instruction without the help of the R0 register so that we can convert R0 register to a read-write register and use for the calculation.
 - ❖ Use busses rather than using many wires
 - ❖ Developing the nanoprocessor in a way that each instruction uses a single clock cycle to execute.
 - ❖ Create Adder and Subtractor in the same unit
 - ❖ Designing the MUX using VHDL conditional statements rather than using four 8-to-1 multiplexers or basic logic gates. It is much easier and less complex.
 - ❖ This nanoprocessor can execute mathematical operations in the range of -8 to $+7$. Therefore, the nanoprocessor should be optimized in a way that any value larger than $+7$ or less than -8 considered as an overflow.
 - ❖ The nanoprocessor, zero flags will be raised only when an ADD instruction is executed.

Resource Consumption (LUT/FF counts):

1. Slice Logic

Site Type	Used	Fixed	Available	Util%
Slice LUTs*	45	0	20800	0.22
LUT as Logic	45	0	20800	0.22
LUT as Memory	0	0	9600	0.00
Slice Registers	53	0	41600	0.13
Register as Flip Flop	53	0	41600	0.13
Register as Latch	0	0	41600	0.00
F7 Muxes	0	0	16300	0.00
F8 Muxes	0	0	8150	0.00

7. Primitives

Ref Name	Used	Functional Category
FDRE	53	Flop & Latch
LUT4	22	LUT
LUT5	18	LUT
OBUF	17	IO
LUT6	11	LUT
LUT3	10	LUT
CARRY4	8	CarryLogic
LUT2	2	LUT
IBUF	2	IO
LUT1	1	LUT
BUFG	1	Clock

Contribution:

Everyone	Nanoprocessor Assemble
Ranathunga N. D. (200517U)	Instruction Decoder NEG Instruction optimization Debugging
Keerthichandra H. M. P. M. (200304N)	Program Counter Program ROM
Marasinghe M. M. R. S. (200382A)	K-way b-bit MUX MUX optimization
Vihidun D. P. T. (200682T)	ADD/SUB Unit ADD/SUB Optimization
Marium M. S. S. (200384G)	3-bit adder Simulations for all components